

LAB 1 Submission


Board Top:

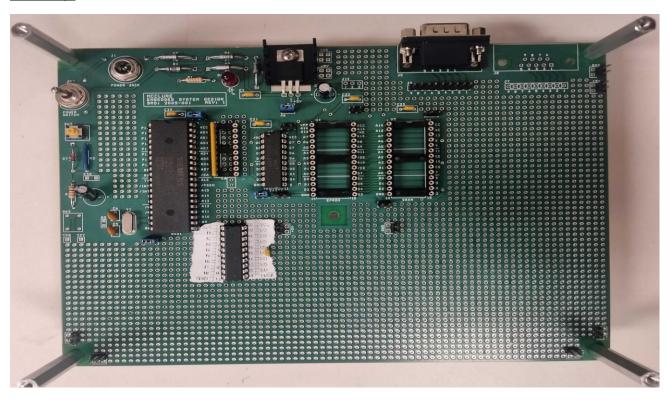


Board Bottom:

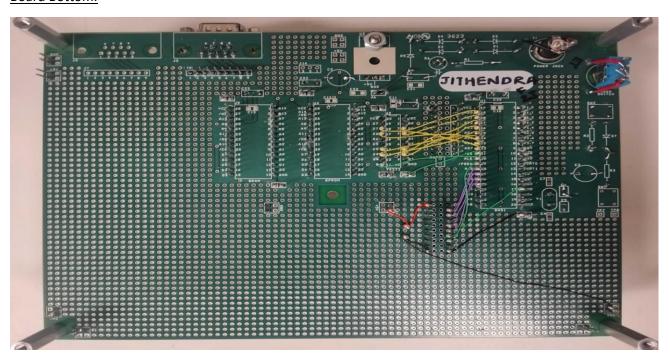


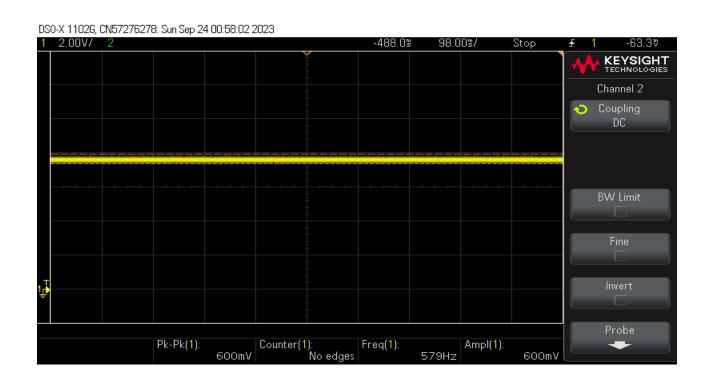
Voltage values at regulator input and output:



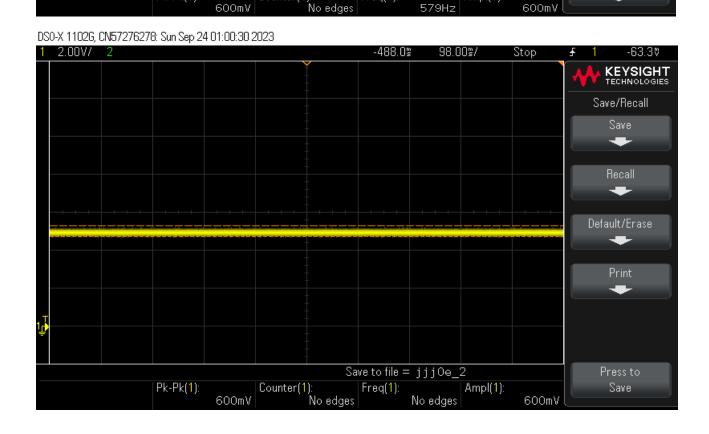

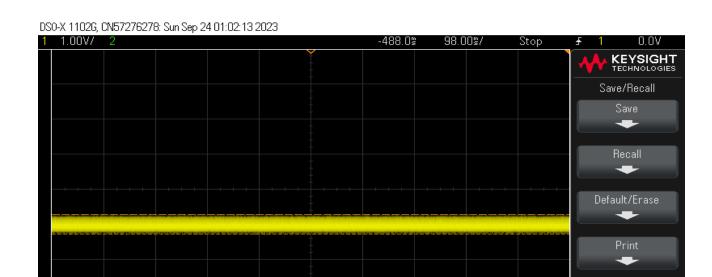Voltage between VCC and GND at top and bottom of MCU:



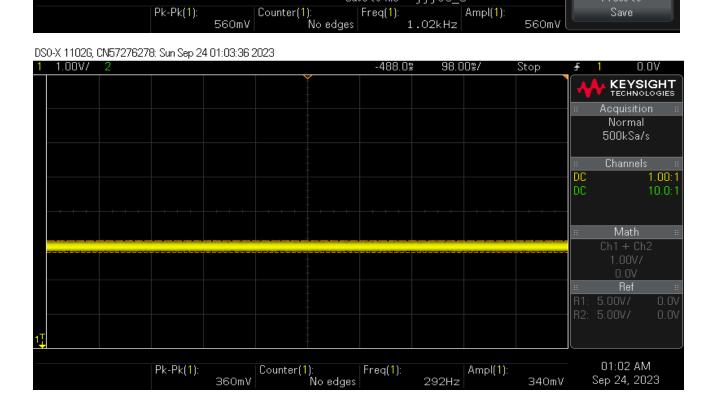

Save to file = jjj0e_3


Freq(1):


Ampl(1):

Save


Voltage at Reset and ALE pin at the time of reset:

Pk-Pk(1):

 

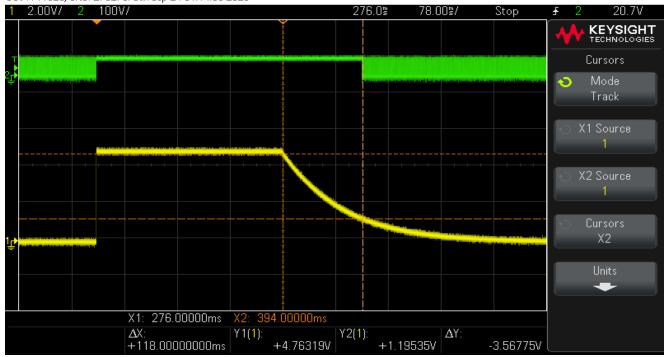

Clock frequency measured at ALE:

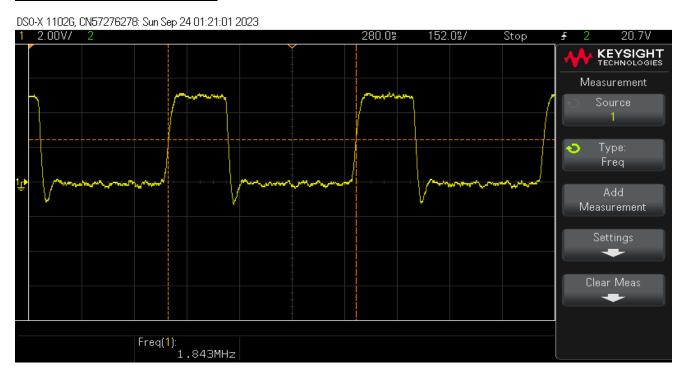

SPLD output measured at logic port application:

